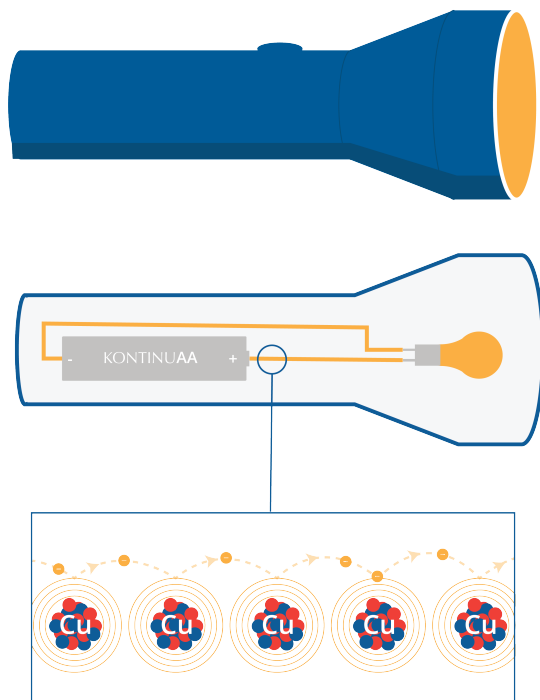


Introduction to Electricity


What happens when you turn on a flashlight? The battery in the flashlight acts as an electron pump. The electrons flow through the wires to the lightbulb (or LED). As the electrons pass through the lightbulb, they excite the molecules within, which gives off light and heat. (LEDs also give off light and heat, but they give off a lot less heat.) Then the electrons return to the battery to be pumped around again.

When electricity is flowing through a copper wire, the protons and neutrons of the copper stay put while the electrons jump between the atoms on their way from the battery to the lightbulb and back again.



In some materials, like copper and iron, electrons are loosely bound to their nuclei, forming a sea of electrons, which allows energy to flow. These are good *electrical conductors*. In other materials, like glass and plastic, electrons don't leave their nuclei easily. Thus, they are terrible electrical conductors – we call them *electrical insulators*. For example, the

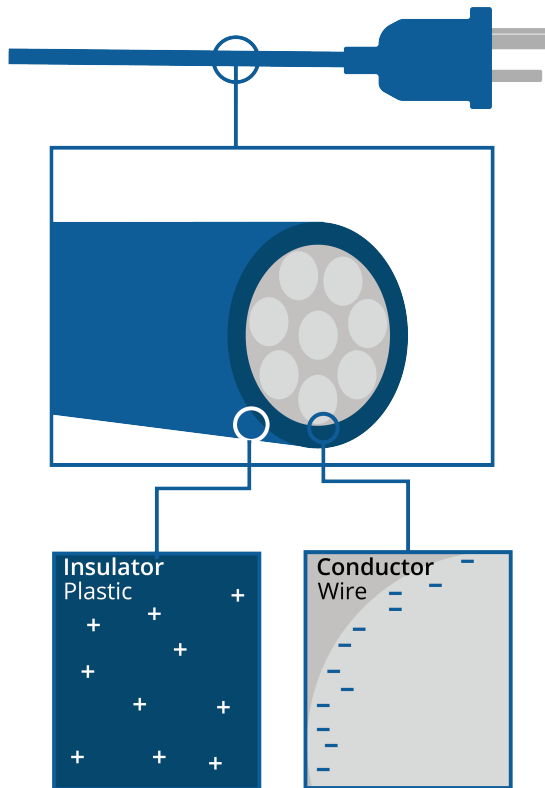plastic around a wire is electrical insulation.



1.1 Units


Electrons are very small, so to study them, scientists came up with a unit that represents *a lot* of electrons. 1 *coulomb* is about 6,241,509,074,460,762,608 electrons. When 5 coulombs enter one end of the wire every second (and simultaneously 5 coulombs exit the other end), we say “This wire is carrying 5 amperes of current.”

(Truthfully, we usually shorten ampere to just “amp”. This is sometimes a little awkward because we often shorten the word “amplifier” to “amp”. You should be able to tell which is which from the context.)

If you look at the circuit breakers or fuses for your home’s electrical system, you’ll see that each one is rated in amps. For example, maybe the circuit that supplies power to your kitchen has a 10 amp circuit breaker. If for some reason, more than 10 amps tries to pass through that wire, the circuit breaker will turn off the whole circuit.

When it is on, your flashlight pushes about 1 amp of current through the lightbulb(When

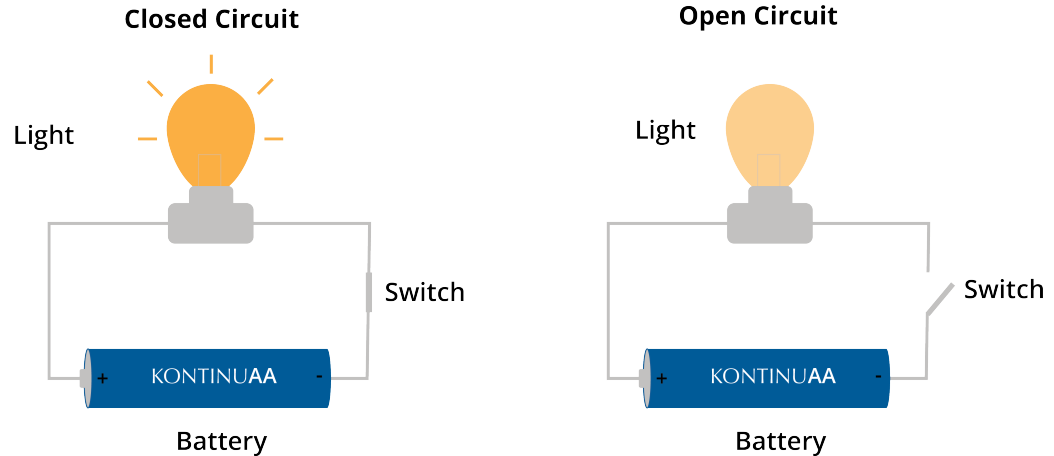
it is off, there is no current in the lightbulb).




The lightbulb creates *Resistance* that the current pushes through. Think of it like plumbing: The current is the amount of water passing through a pipe. The resistance is something that tries to stop the current – like a ball of hair. The battery is what allows the current to push through the resistance; we call that pressure *voltage*.

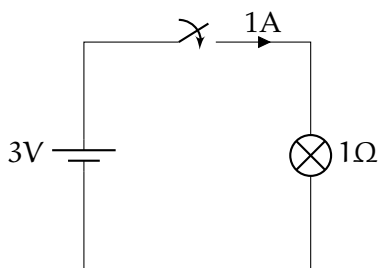1.2 Circuit Diagrams

Here is a circuit diagram of your flashlight:



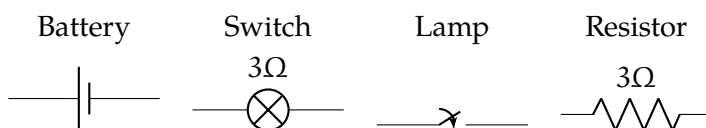The lines are wires. The symbols that we will use:



The battery pushes the electrons from one end and pulls them back in at the other, so the circuit must go around in a circle for the current to flow. This is why the current stops flowing when the switch breaks the circuit.

You can think of a switch as having zero resistance when it is closed and infinite resistance when it is open.

For our purposes, a lamp is just a resistor that gives off light.

1.3 Ohm's Law

Resistance is measured in *ohms*, and we use a Greek capital omega for that: Ω

Voltage is measured in *volts*.

Ohm's Law

Whenever a voltage V is pushing a current I through a resistance of R , the following is true:

$$V = IR$$

where V is in volts, I is in amps, and R is in ohms.

1.4 Power and Watts

Joule's Law

When a current I is passing through a resistance R , the power consumed is

$$W = I^2R$$

where W is in watts, I is in amps, and R is in ohms.

Of course $V = IR$, so we can extend this to:

$$W = I^2R = IV = \frac{V^2}{R}$$

Your flashlight's batteries provide about 3 volts. How much battery power is the flashlight

using when it is on? The power (in watts) produced by the battery is the product of the voltage (in volts) and the current (in amps). So your flashlight is giving off $3\text{volts} \times 1\text{amp} = 3\text{watts}$ of power. Some of that power is given off as light, some as heat.

A watt is 1 joule of energy per second. We say that a watt is a measure of *power*.

When we talk about how much energy is stored in a battery, we use a unit like a kilowatt-hour. A kilowatt-hour is equivalent to 3.6 million joules.

1.5 Another great use of RMS

In many electrical problems, the voltage fluctuates a lot. For example, the fluctuations in voltage makes the sound that comes out of an audio speaker.

You can use the root-mean-squared of the voltage to figure out the average power your speaker is consuming.

Let's say that the RMS of the voltage you are sending to the speaker is V_{rms} and the resistance of the speaker is R ohms, then the power consumed by the speaker is:

$$P = \frac{V_{\text{rms}}^2}{R}$$

Similarly, if you know the RMS of the current you are pushing through the speaker is I_{rms} , then the power consumed by the speaker is:


$$P = I_{\text{rms}} R$$

1.6 Electricity Dangers

Large amounts of electricity moving through your body can hurt or even kill you. You must be careful around electricity.

However, your body is not a very good conductor, so low-voltage systems (like a flashlight) don't have enough voltage to move significant amounts of current through your body.

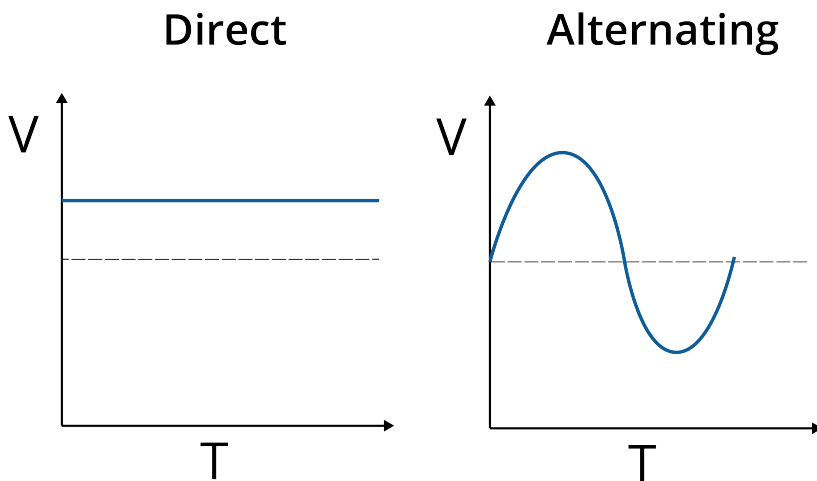However, the electricity in a power outlet has much more voltage. The voltage in these outlets is fluctuating between positive and negative, so we call it *Alternating Current* or AC.



In most countries, the RMS of the voltage between 110 and 240 V. (The peak voltage is always $\sqrt{2}$ times the RMS value. In the US, for example, people say “Our outlets supply 120 V.” They mean that the RMS of the voltage difference between the wire and the earth is 120V. The peak voltage is almost 170V.)

How much current can a human handle? Not much. You can barely feel 1 mA moving through your body, but at 16 mA, your muscles will clench and you won’t be able to relax them – many people die from electrocution because they grab a wire which pushes enough current through their body to prevent them from letting go of the wire. At 20 mA, a human’s respiratory muscles become paralyzed.

The fuse breaker in a house will often allow 20 A to flow through the circuit before it shuts off the power: Always, always, always shut off the power before touching any of the wiring in your house.

While water is actually a mediocre conductor, it can still deliver enough current to kill you. If you see a wire in a puddle, you should not touch the puddle. Interestingly, because of the salt, sea water is more than 100 times better at conducting electricity than the water you drink.

If you hold a wire in each hand, how many Ohms of resistance will your body have? Once it gets past your skin, you will look like a bag of salt water to the electricity. After the skin, your body will have a resistance of about 300Ω . However, the skin is a pretty good insulator. If you have dry, calloused hands, your skin may add a $100,000\Omega$ to the resistance.

This is a draft chapter from the Kontinua Project. Please see our website (<https://kontinua.org/>) for more details.

Answers to Exercises



INDEX

amp or ampere, [2](#)

coulombs, [2](#)

Joule's law, [4](#)

Ohm's law, [4](#)
ohms, [4](#)

resistance, [3](#)

voltage, [3](#)
volts, [4](#)

watts, [5](#)